

Luis Ruiz
5001441817
CPE 300-1001
Final Project

1. The project required us to build a microprocessor. The microprocessor made us apply our knowledge on what we have been learning these past few months and build off of it. The processor itself required us to build a data path and control unit that would decode and execute a set of instruction. In essence the processor is a compiler which grabs a certain amount of instructions and executes the instructions by decoding it using a control unit, the control unit then gives the data path the bits in order to execute the instruction.

Most of the instructions in my control unit require 3 cycles and only a few require 4 cycles. The first cycle is always the Fetch cycle, the 2nd cycle is dedicated to decoding what instruction is to be executed, and 3rd cycle is usually the cycle where the instruction is executed. A 4th cycle is required for instructions such as LDM and STM where a value is being stored into my Accumulator and or the Memory itself.

Instructions to Be Executed

```
000000: LDI A, 5           // Accumulator <- 5
000010: DEC A               //Accumulator <-4
000011: JNZ 000010          //PC <-000010 if Accumulator! =0
000101: INC A                 //Accumulator<-1
000110: STM 001111, A         //RAM [001111] <-1
001000: STA 0, A              //RF [000] <-1
001001: ADD A, 0              //A <- RF [000] +1
001010: STM 010000, A        //RAM [010000] <- 2
001100: HALT                 //STOP
```


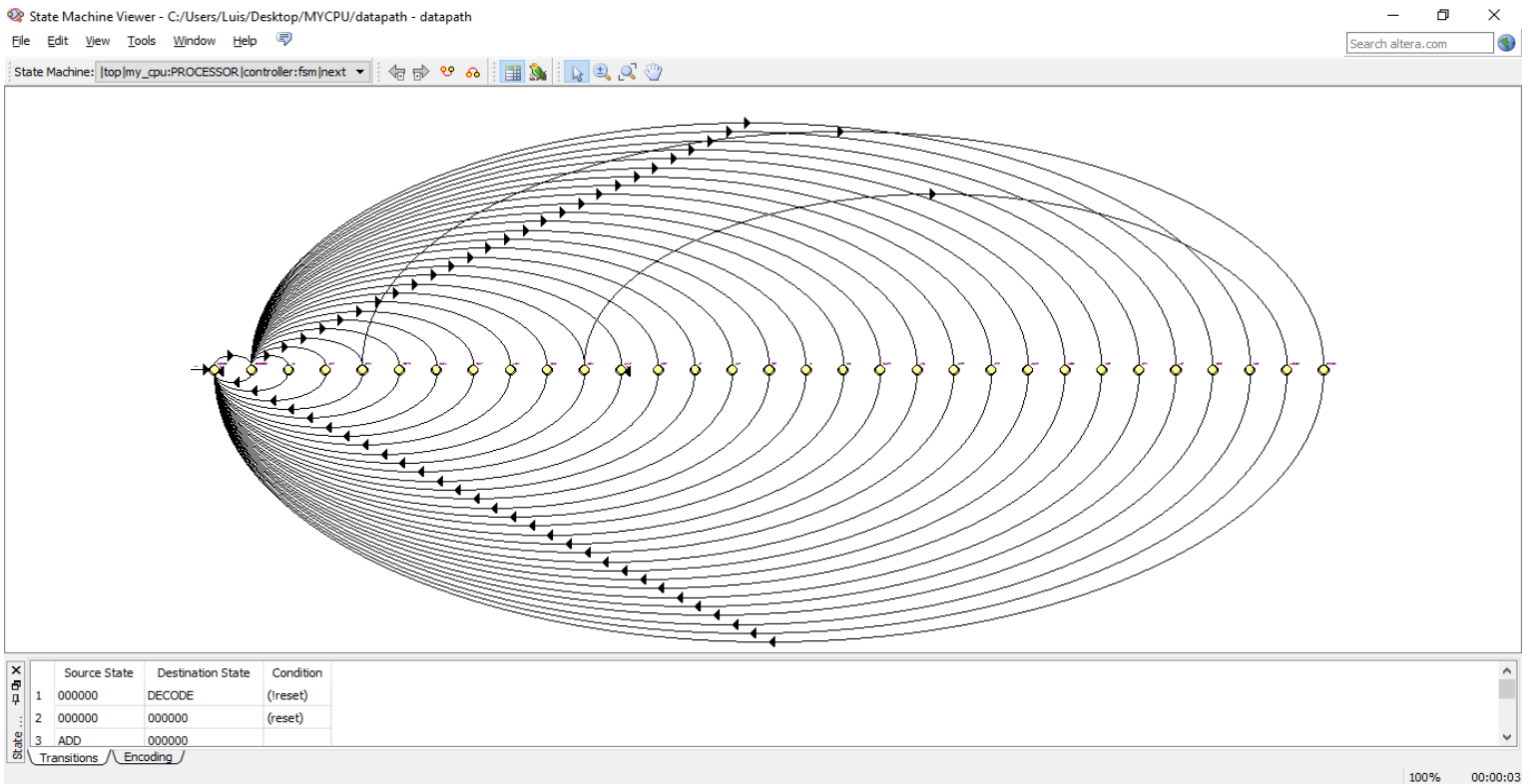


Figure 1: FSM Schematic

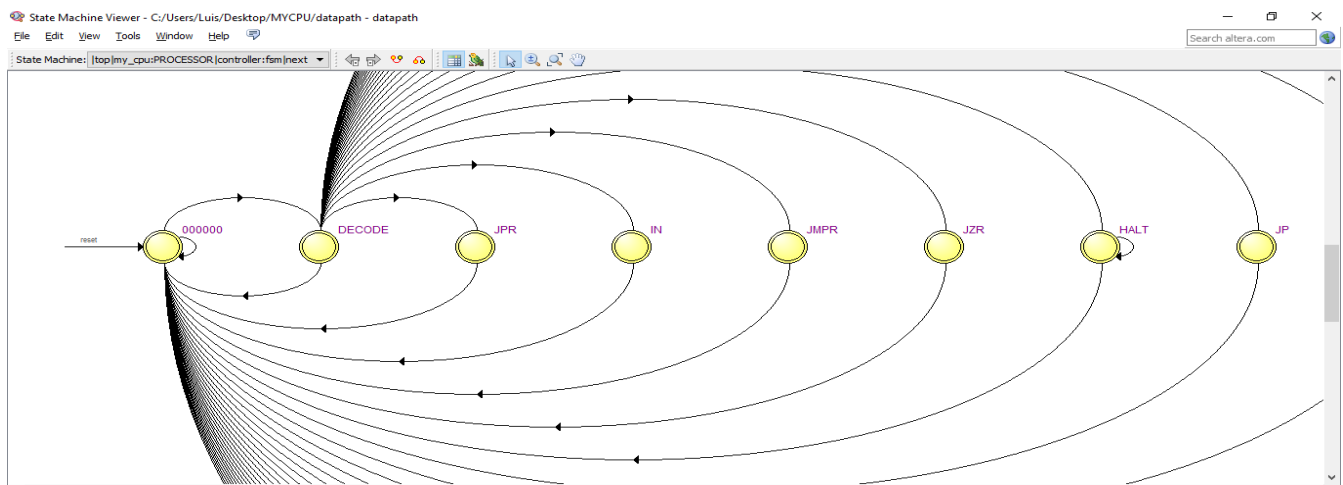

2. Describe the control unit design.
 - a) How many instructions are decoded and the ALUSel and ShiftSel encoded?
 - i. The number of instructions that were decoded were 27 distinct instructions. Each instruction was dedicated a specific state and the control signals were given at the present state.
 - b) Whether the control circuit is FSM or Clock counter+ decoder+ Combination
 - i. 29 states, one for fetch and decode and then 27 distinct states, one for each instruction. When the code started the instructions were initially stored into my Memory. Once stored into Memory the code was fetched on the first clock pulse and then decoded. Once it was decoded our present state was the instruction and this is where the controls to the data path are given.

- The Test bench I created really only generates a clock pulse and ends when all my instructions have been fully executed. The Test bench display a message saying it has finished when it has all the expectations have been met. The screen shots provided will display the values that were stored in the memory location 001111, 010000, and also the content of what R [0] holds.

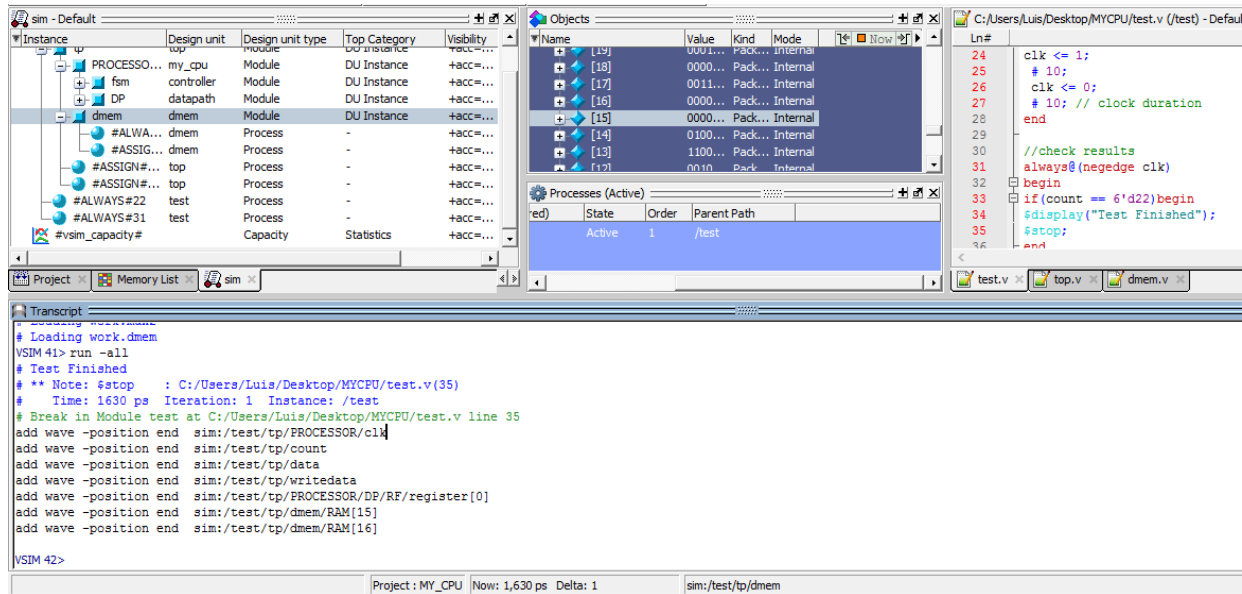


Figure 4: Shows the instruction that were added to display on the wave form

 


Figure 5: Shows the wave form, from model slim

- The clock requires a period 8.50ns in order to have a positive slack of 0.113ns. This means that the longest instruction took roughly about 8.35 ns in order to complete thus giving us a positive slack.

ps	delta	list/tp/count	/test/tp/data	/test/tp/dmem/RAM[15]	/test/tp/dmem/RAM[16]	/test/tp/writedata	/test/tp/PROCESSOR/DP/RF/register[0]
500	+3	000100	10000000	00000011	xxxxxxx	00010000	00010000
540	+3	000101	00000011	00000011	xxxxxxx	00010000	00010000
580	+5	000101	00000011	00000010	xxxxxxx	00010000	00010000
600	+3	000110	00000011	00000010	xxxxxxx	00010000	00010000
640	+3	000011	11100010	00000010	xxxxxxx	00010000	00010000
660	+3	000100	10000000	00000010	xxxxxxx	00010000	00010000
700	+3	000101	00000011	00000010	xxxxxxx	00010000	00010000
740	+5	000101	00000011	00000001	xxxxxxx	00010000	00010000
760	+3	000110	00000011	00000001	xxxxxxx	00010000	00010000
800	+3	000011	11100010	00000001	xxxxxxx	00010000	00010000
820	+3	000100	10000000	00000001	xxxxxxx	00010000	00010000
860	+3	000101	00000011	00000001	xxxxxxx	00010000	00010000
900	+5	000101	00000011	00000000	xxxxxxx	00010000	00010000
920	+3	000110	00000011	00000000	xxxxxxx	00010000	00010000
960	+3	000111	11100001	00000000	xxxxxxx	00010000	00010000
980	+3	001000	01000000	00000000	xxxxxxx	00010000	00010000
1020	+3	001001	00001111	00000000	xxxxxxx	00010000	00010000
1060	+5	001001	00001111	00000001	xxxxxxx	00010000	00010000
1080	+3	001010	00001111	00000001	xxxxxxx	00010000	00010000
1120	+2	000000	01010000	00000001	xxxxxxx	00010000	00010000
1120	+3	001111	00010000	00000001	xxxxxxx	00010000	00010000
1140	+2	001011	00000000	00000001	xxxxxxx	00000001	00010000
1160	+3	001100	00100000	00000001	xxxxxxx	00000001	00010000
1200	+3	001101	11000000	00000001	xxxxxxx	00000001	00010000
1260	+3	001110	01000000	00000001	xxxxxxx	00000001	00010000
1300	+2	001110	01000000	00000001	00000001	00000001	00010000
1320	+3	001111	00000001	00000001	00000001	00000001	00010000
1360	+5	001111	00000001	00000010	00000001	00000001	00010000
1380	+3	010000	00010000	00000010	00000001	00000001	00010000
1420	+2	001111	00000001	00000010	00000001	00000001	00010000
1420	+3	010000	00010000	00000010	00000001	00000001	00010000
1440	+2	010001	00110000	00000010	00000001	00000001	00000010
1460	+3	010010	00001111	00000010	00000001	00000001	00000010
1500	+3	010011	00010000	00000010	00000001	00000001	00000010

add list -width 16 /test/tp/count

add list /test/tp/data

add list /test/tp/writedata

add list {/test/tp/PROCESSOR/DP/RF/register[0]}

add list {/test/tp/dmem/RAM[15]}

add list {/test/tp/dmem/RAM[16]}

configure list -usestrobe 0

configure list -strobestart {0 ps} -strobeperiod {0 ps}

configure list -usesignaltrigger 1

configure list -delta all

configure list -signalnamewidth 0

configure list -datasetprefix 0

configure list -namelimit 5

Figure 6: List which also displays R[0] Mem 010000,001111

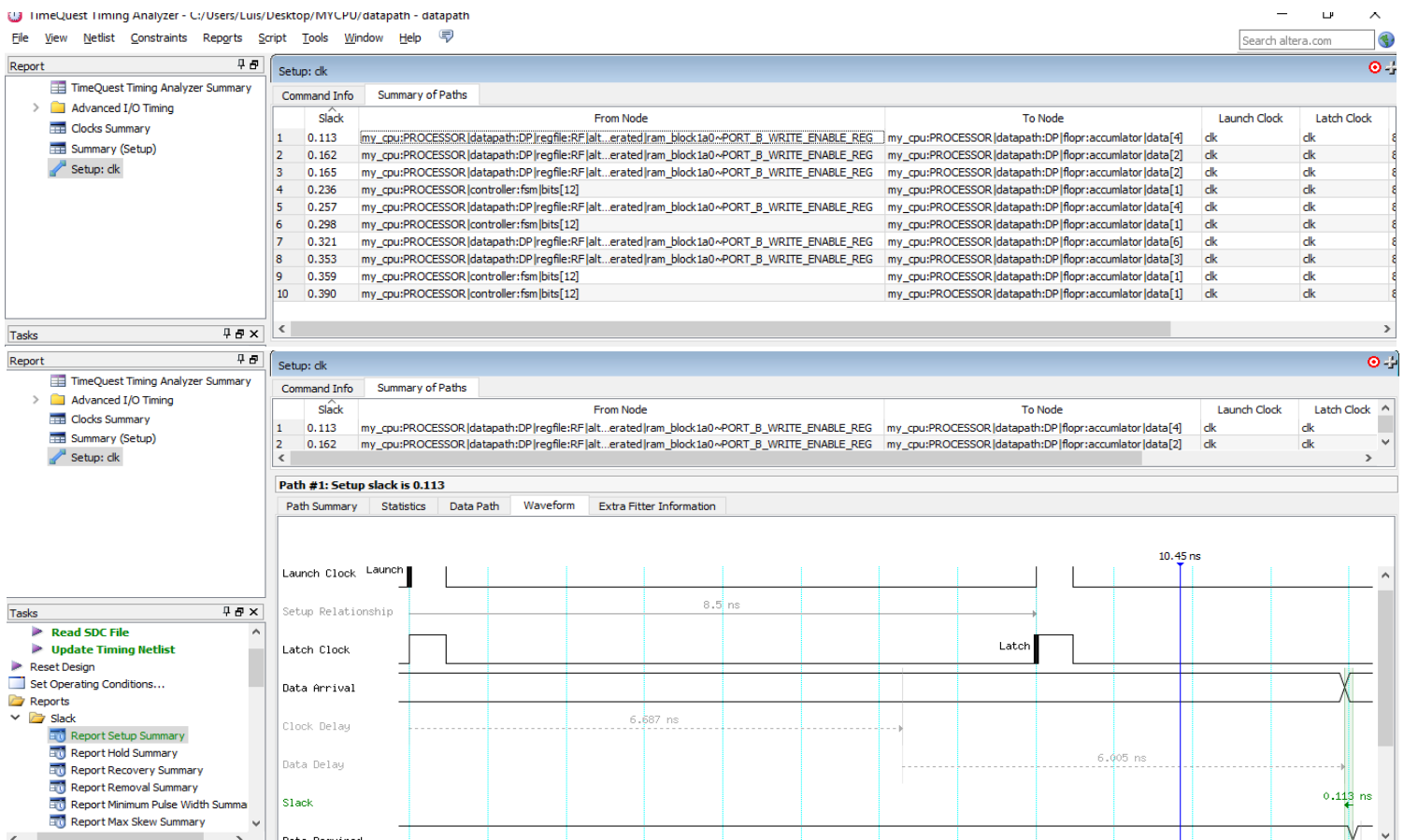


Figure 7: Time Quest Analysis

7. The only hiccup I had throughout the project were instructions that had two bytes. For some reason I have to place the 2nd bytes twice in order for it to work you will notice it in my memfile.dat. My guess was it required a delay in order to keep the 2nd byte longer.